
 


Introduction into Electronics

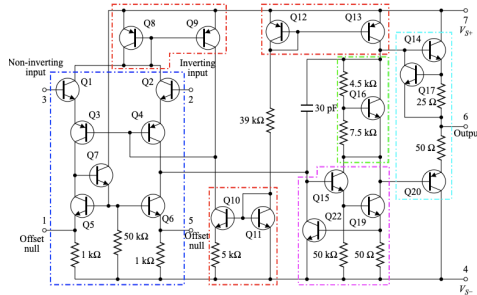
- (1) Reminder: Electrical circuits
- (2) Analog electronics
- (3) Digital electronics
- (4) Circuit analysis, circuit topologies




(1) Reminder: Electrical circuits

Basic elements


Power source:

 

DC voltage source:

 

DC current source:

 


AC source:

$$U(t) = U_0 \sin(\omega t)$$


$$\hat{U} = U_{eff} = U_0 / \sqrt{2}$$




Resistance:

 

$$U = R \cdot I.$$

 


Capacitance:

 

$$Q = C \cdot U \quad i(t) = \frac{dq}{dt} = C \cdot \frac{du}{dt}$$


Inductance:

 


$$u(t) = L \frac{di}{dt}$$

AC resistance


Resistance:

 

$$I_R = \frac{U_R}{R}$$

 


Capacitance:

 


$$\hat{U}_C = \hat{I}_C X_C$$

$$X_C = \frac{1}{\omega_a C}$$

 


Inductance:

 

$$\hat{U}_L = \hat{I}_L X_L$$


$$X_L = \omega_a L$$

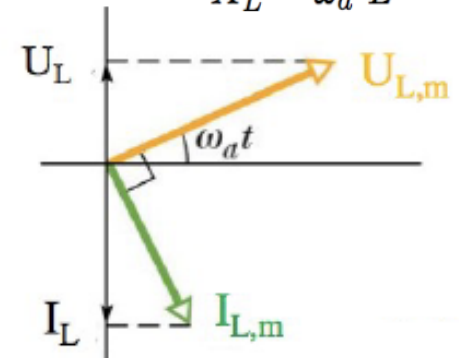

Networks (more later)


Junction rule:

$$\sum_{k=1}^n I_k = 0$$


 


Loop rule

$$\sum_{k=1}^n U_k = 0$$

 

Impedance in AC circuits

  


Impedance Z :

$$\hat{I} = \frac{\hat{U}}{Z}$$


$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Resistance in series:

 


$$R_{\text{total}} = R_s = R_1 + R_2 + \dots + R_n$$

Resistance in parallel:

 


$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

Low pass

 

high pass

 


$$X_C = \frac{1}{\omega_a C}$$



(2) Analog electronics

Diode: pn junction and biasing


 


No bias voltage

Forward Bias: Depletion zone reduced

Reverse Bias: Depletion zone increased

  Electrons cross the junction from n to p type → depletion zone, barrier voltage



Current-voltage characteristic

Diode: forward biasing

Ideal diode (forward bias):

$$I(U) = I_S \cdot \left(e^{\frac{U}{U_T}} - 1 \right)$$

I_S : leakage current $\approx 1\text{-}100 \mu\text{A}$

$U_T = kT/e \approx 40 \text{ mV}$


Real diode (forward bias):

$I(U)$ only > 0

for $U > \text{Barrier Voltage}$ ($\approx 0.3\text{-}0.8\text{V}$)


Differential resistance:

$$r = \frac{dI}{dU}$$

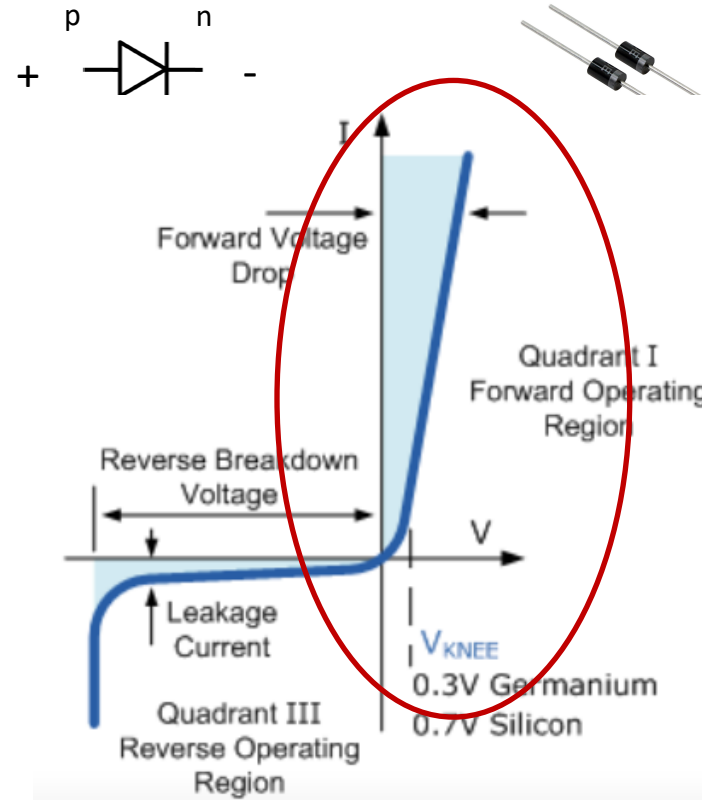

Current-voltage characteristic


Zener diodes: reverse biasing

 

Conventional diodes will typically be destroyed if operated with large reverse-bias voltages.


But a Zener diode is designed to be operated with reverse bias.

 Resistance breaks down at the Zener voltage: tunneling of electrons
From the p-type valence band into the n-type conduction band
→ Voltage stabilizer, reference voltage




Circuits with diodes (1)


Half-wave rectifier

 


Blocks negative half waves

 

 Half-wave rectifier with smoothing capacitor




Half waves smoothed

 

Circuits with diodes (2)


Full-wave Bridge rectifier

 

Diodes are arranged such that the positive pole is always connected to the same point.


--> Inverts negative half waves

 Bridge rectifier with smoothing capacitance



Voltage regulation/limitation:

 If the initial voltage becomes larger than the Zener voltage the Zener current increases \rightarrow resistance drops




Transistors

- Active, controllable semiconductor devices.
- Amplify and switch signals and power
- Main types:


- **Bipolar junction transistor (BJT)**

 - here: **npn transistor**
- pnp transistor: works in an analogous manner




- **Field Effect Transistor (FET)**

 - MOSFET: **NMOS/PMOS**
- CMOS: combines NMOS and PMOS




Contemporary Integrated Circuits (IC) are in general not build from discrete transistors but need to understand the transistor principle to understand IC


Bipolar Junction Transistor

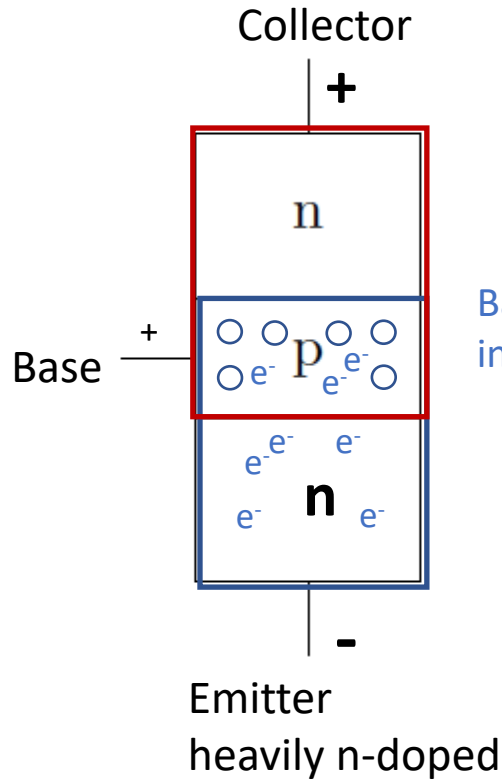

 Base-Emitter diode: operated in forward direction




Bipolar Junction Transistor

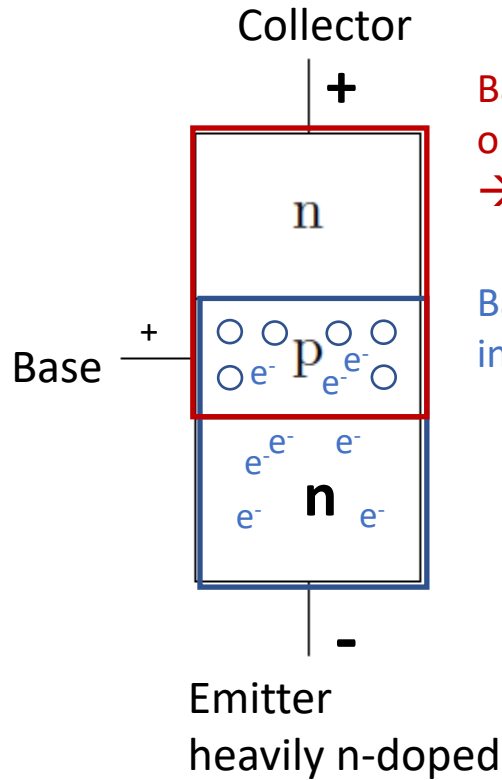


Base-Collector diode:
operated in reverse bias
→ “leakage” collector current I_C

 Base-Emitter diode: operated
in forward direction




Bipolar Junction Transistor

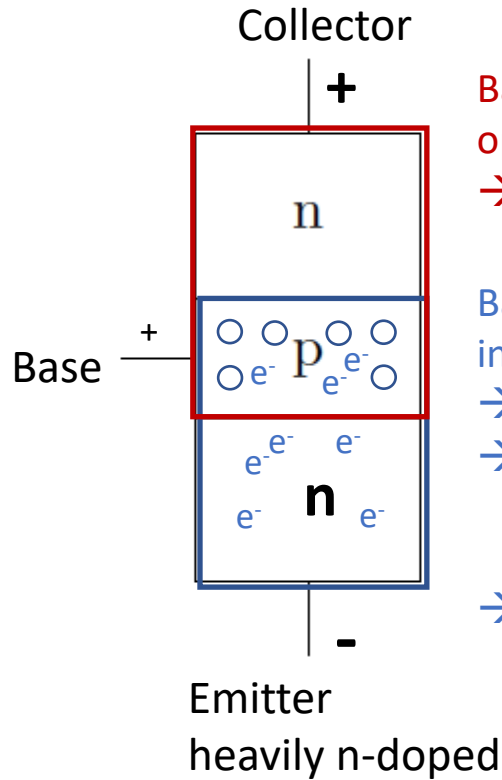


Base-Collector diode:
operated in reverse bias
→ “leakage” collector current I_C

 Base-Emitter diode: operated
in forward direction
→ electrons drift into the base
→ some electrons reach the
p-n transition region of the
Base-Collector diode
→ increase collector current I_C




Bipolar Junction Transistor

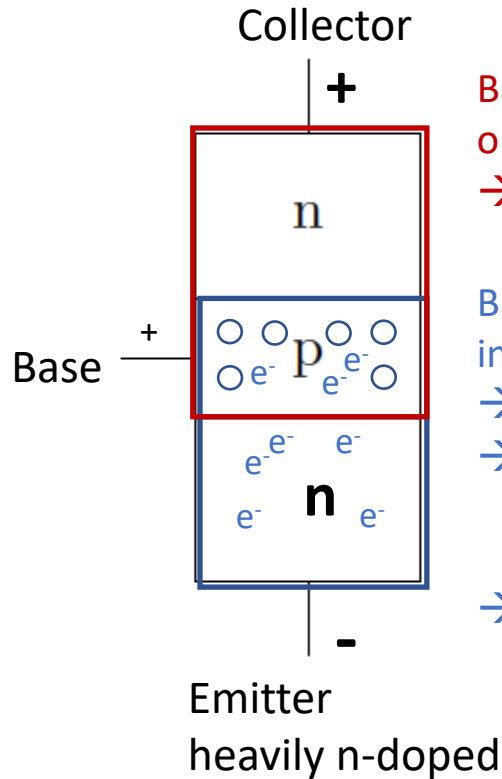

Base-Collector diode:
operated in reverse bias
→ “leakage” collector current I_C

 Base-Emitter diode: operated
in forward direction
→ electrons drift into the base
→ some electrons reach the
p-n transition region of the
Base-Collector diode
→ increase collector current I_C





$$I_E = I_C + I_B$$

$$U_{CE} = U_{CB} + U_{BE}$$

$I_B/U_{BE} \rightarrow \text{control} \rightarrow I_C$


npn BJT: characteristics (1)

Input characteristics

 
 


npn BJT: characteristics (1)

Input characteristics

 

Output characteristics

 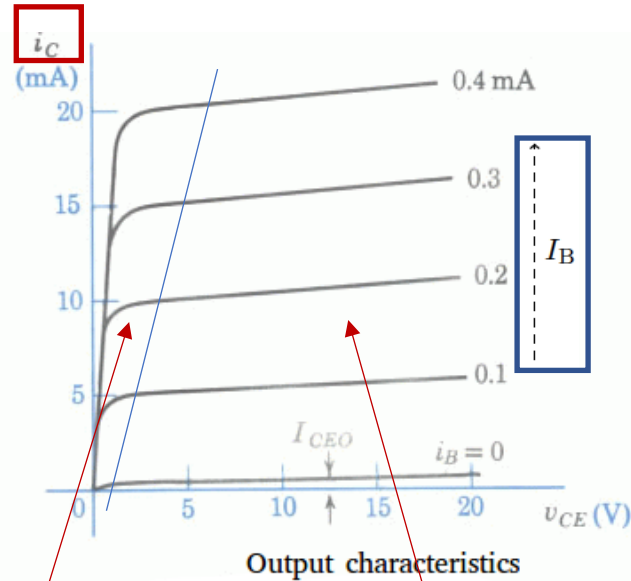

Saturation region:


Small changes in U_{CE} lead to large change in I_C
→ switches etc.

Active region:

Small change in base current I_B lead to large change in collector current, nearly independent of U_{CE}
→ Current amplification etc.


npn BJT: characteristics (2)

- working point in active region

 

Selecting the working point

Example circuit

 

(Calculation: see later)

Voltage divider biasing

The voltage U_B across R_2 forward-biases the BE junction


$$U_B = U_0 \cdot \frac{R_2}{R_1 + R_2} - I_B \cdot \frac{R_1 R_2}{R_1 + R_2}$$

If R_1, R_2 are sufficiently small, the base current does not impact the base voltage

$$I_B \cdot R_1 \ll U_0 \quad \rightarrow \quad U_B \approx U_0 \cdot \frac{R_2}{R_1 + R_2}$$

Selecting the working point

Example circuit

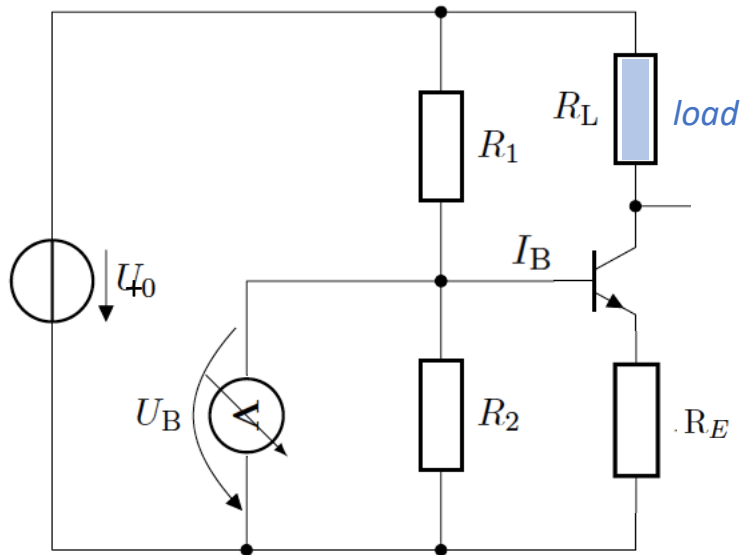

Voltage divider biasing

The voltage U_B across R_2 forward-biases the BE junction

$$U_B = U_0 \cdot \frac{R_2}{R_1 + R_2} - I_B \cdot \frac{R_1 R_2}{R_1 + R_2}$$

If R_1, R_2 are sufficiently small, the base current does not impact the base voltage


$$I_B \cdot R_1 \ll U_0 \quad \rightarrow \quad U_B \approx U_0 \cdot \frac{R_2}{R_1 + R_2}$$

Stabilizing WP by adding emitter resistance R_E

Reduces U_{BE} if base current I_B becomes too large.

Selecting the working point

Example circuit

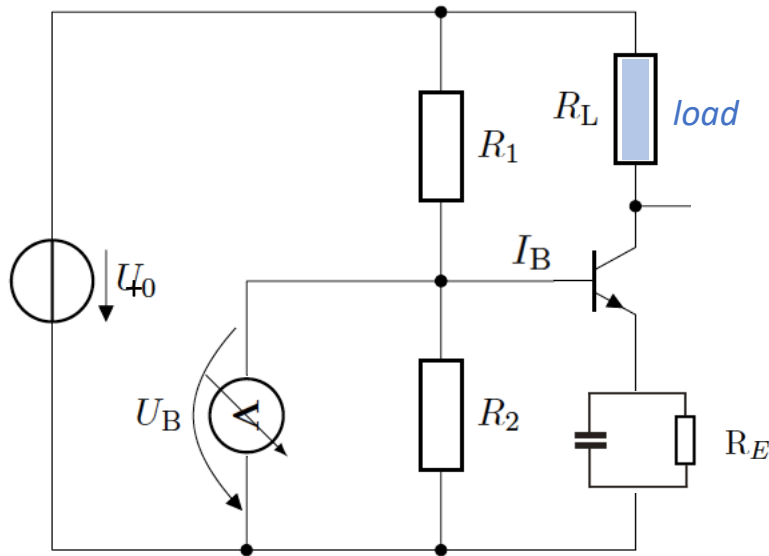

Voltage divider biasing

The voltage U_B across R_2 forward-biases the BE junction

$$U_B = U_0 \cdot \frac{R_2}{R_1 + R_2} - I_B \cdot \frac{R_1 R_2}{R_1 + R_2}$$

If R_1, R_2 are sufficiently small, the base current does not impact the base voltage

$$I_B \cdot R_1 \ll U_0 \quad \rightarrow \quad U_B \approx U_0 \cdot \frac{R_2}{R_1 + R_2}$$

Stabilizing WP by adding emitter resistance R_E

Reduces U_{BE} if base current I_B becomes too large.

Effect on AC signal can be mitigated by adding a capacitor in parallel

$\rightarrow R_E \parallel R_C$ reduced for high frequencies, $R \approx R_E$ for low frequencies

FET


BJT not suited for Integrated Circuits (IC): base currents would overheat the IC

→ use FETs: similar operation as with BJT but:


- controlled with negligible currents
- smaller area
- transfer characteristics more linear
- less noise

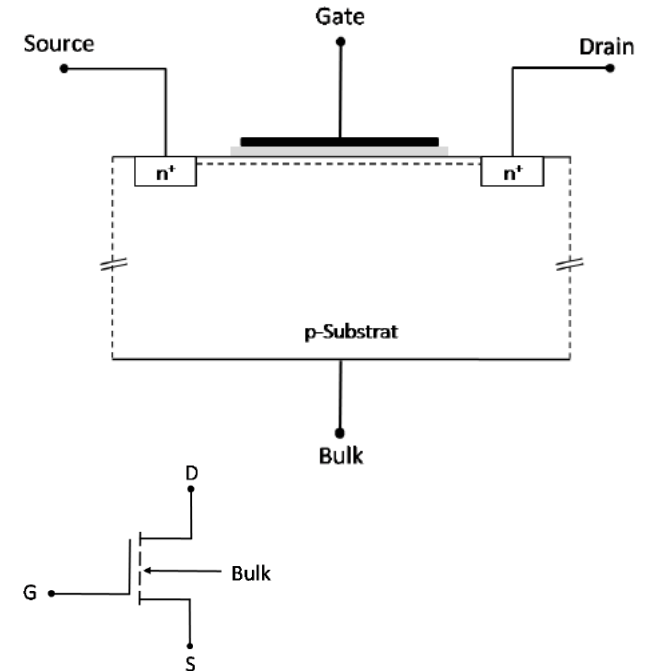Example n-channel MOSFET (Metal-Oxide-Silicon FET):

- p-doped substrate
- n-doped channels: Source, Drain
- Gate isolated from substrate by e.g. SiO_2
 - → no Gate-Source/Drain currents




N-channel MOSFET: operation

 


- No source drain current

N-channel MOSFET: operation


 


- No source drain current

 


- Electrons from p-doped substrate drawn towards positively charged gate
- → channel allows for S-D current I_D

N-channel MOSFET: operation

  

- No source drain current


 
- Electrons from p-doped substrate drawn towards positively charged gate
- → channel allows for S-D current I_D



Typically smaller transconductance than BJT (output current /input voltage)

Operational amplifier (op amp)

 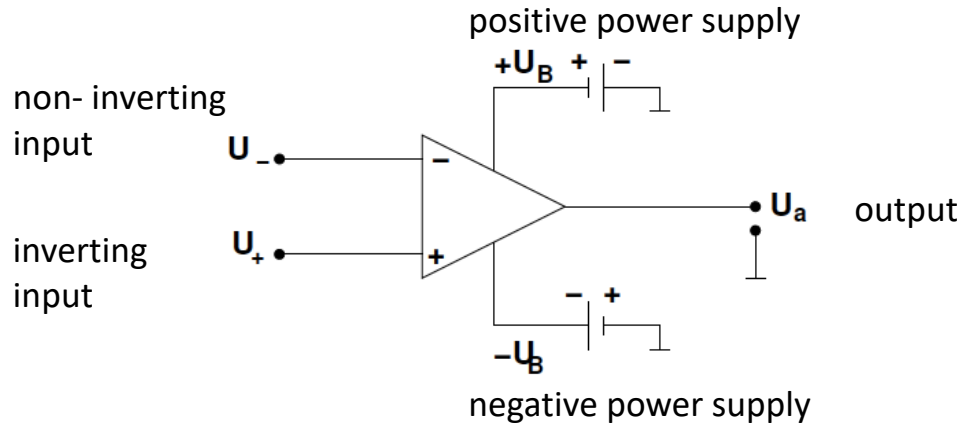
Difference amplifier with two inputs and one output



Characteristics:

- Output voltage proportional to the difference between the input voltages: very high amplification ($> 10000-100000$)
- If used with negative feedback (U_a connected with U_-) the op amp regulates $U_+ = U_-$ [1]
- Negligible input current (into the op amp) [2]
- The maximum output voltage is the power supply voltage


$$U_a = v_0 \cdot (U^+ - U^-)$$

 

negative feedback

Op amp circuits

Inverting amplifier

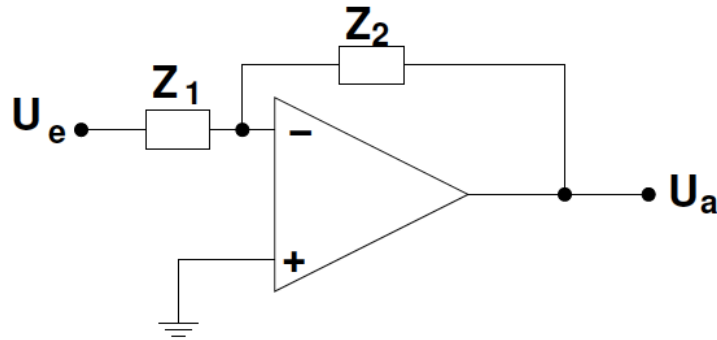


$$[2] \rightarrow I_1 = \frac{U_e - U^-}{Z_1} = \frac{U^- - U_a}{Z_2} = I_2$$

$$[1] \rightarrow U^- = 0 \text{ V (virtual ground)}$$

$$\rightarrow U_a = -\frac{Z_2}{Z_1} U_e$$

- If used with negative feedback (U_a connected with U^-) the op amp regulates $U^+ = U^-$ [1]
- Negligible input current (into the op amp) [2]

Non-inverting amplifier

 


Negative feedback from voltage divider:

$$[1] \rightarrow U_e = U^- = \frac{Z_1}{Z_1 + Z_2} U_a$$

$$\rightarrow U_a = \left(\frac{Z_2}{Z_1} + 1 \right) U_e$$

Op amp circuits

Differential amplifier

 

$$[1] U_- = U_+ = U$$

$$[2] I_1 = \frac{U_1 - U}{R_1} = I_2 = \frac{U - U_a}{R_2}$$


$$\rightarrow \frac{U_1 R_2}{R_1} - \frac{U R_2}{R_1} = U - U_a$$

$$\rightarrow U_a = U \frac{R_2 + R_1}{R_1} - U_1 \frac{R_2}{R_1} (*)$$

- If used with negative feedback (U_a connected with U_-) the op amp regulates $U_+ = U_-$ [1]
- Negligible input current (into the op amp) [2]

Op amp circuits

Differential amplifier

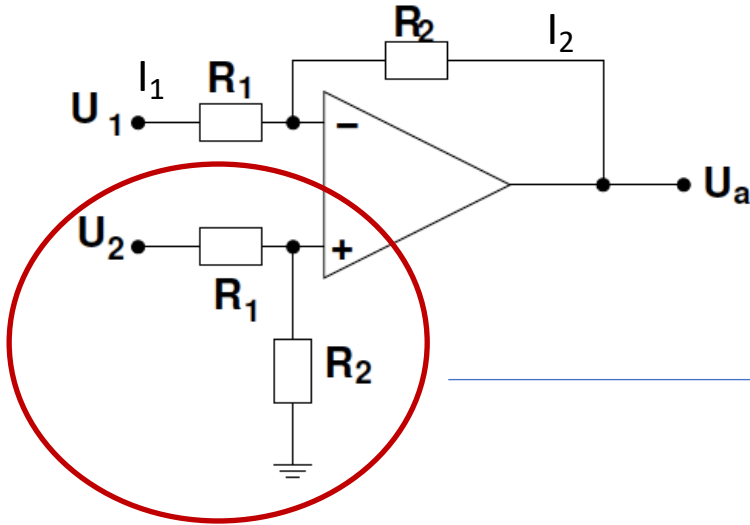

$$[1] \quad U_- = U_+ = U$$

$$[2] \quad I_1 = \frac{U_1 - U}{R_1} = I_2 = \frac{U - U_a}{R_2}$$

$$\rightarrow \frac{U_1 R_2}{R_1} - \frac{U R_2}{R_1} = U - U_a$$


$$\rightarrow U_a = U \frac{R_2 + R_1}{R_1} - U_1 \frac{R_2}{R_1} \quad (*)$$

$$U = U_2 \frac{R_2}{R_1 + R_2} \quad (\text{voltage divider}) \quad (**)$$

- If used with negative feedback (U_a connected with U_-) the op amp regulates $U_+ = U_-$ [1]
- Negligible input current (into the op amp) [2]

Op amp circuits

Differential amplifier

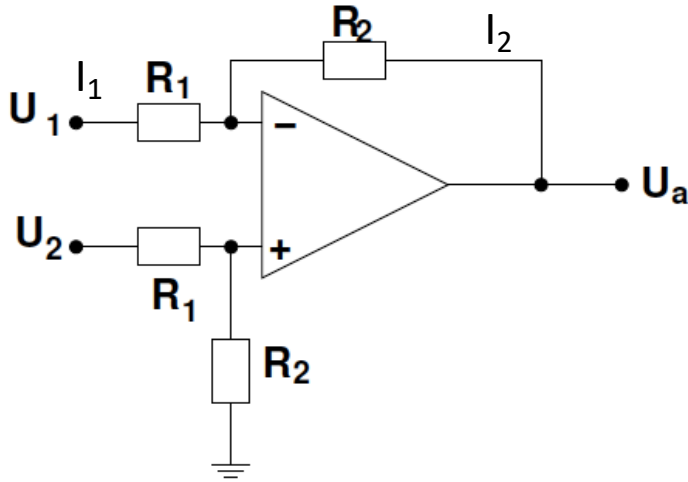

$$[1] \quad U_- = U_+ = U$$

$$[2] \quad I_1 = \frac{U_1 - U}{R_1} = I_2 = \frac{U - U_a}{R_2}$$

$$\rightarrow \frac{U_1 R_2}{R_1} - \frac{U R_2}{R_1} = U - U_a$$

$$\rightarrow U_a = U \frac{R_2 + R_1}{R_1} - U_1 \frac{R_2}{R_1} \quad (*)$$

$$U = U_2 \frac{R_2}{R_1 + R_2} \quad (\text{voltage divider}) \quad (**)$$

(**) in (*)


$$\rightarrow U_a = U_2 \frac{R_2}{R_1 + R_2} \frac{R_1 + R_2}{R_1} - U_1 \frac{R_2}{R_1}$$

$$\rightarrow U_a = \frac{R_2}{R_1} (U_2 - U_1)$$

- If used with negative feedback (U_a connected with U_-) the op amp regulates $U_+ = U_-$ [1]
- Negligible input current (into the op amp) [2]

Op amp circuits

Integrator

 


Virtual ground offset by input current
→ op amp passes a current that charges the capacitor to maintain the virtual ground

$$I_R = \frac{U_e}{R} \approx I_C$$

Op amp circuits

Integrator

 

Virtual ground offset by input current
→ op amp passes a current that charges the capacitor to maintain the virtual ground

$$I_R = \frac{U_e}{R} \approx I_C$$


Capacitor equation:

- Differential: $I = C \frac{dU}{dt}$

- Integrated: $U = \frac{1}{C} \int I dt$ (*)

Op amp circuits

Integrator

 

Capacitor equation:

- Differential: $I = C \frac{dU}{dt}$

- Integrated: $U = \frac{1}{C} \int I dt$ (*)

Virtual ground offset by input current
→ op amp passes a current that charges the capacitor to maintain the virtual ground

$$I_R = \frac{U_e}{R} \approx I_C$$


with(*):

$$U_a = -\frac{1}{RC} \int_0^t U_e dt$$

→ The output voltage is proportional to the time integrated input voltage

Op amp circuits

Schmitt trigger: positive feedback

 


$$U_a = v_0 \cdot (U^+ - U^-)$$

If U_a rises, the difference between U_e and U_+ will rise. This causes U_a to rise even further until maximum output voltage (given by the power supply voltage) is reached

Op amp circuits


Schmitt trigger: positive feedback

 

$$U_a = v_0 \cdot (U^+ - U^-)$$

If U_a rises, the difference between U_- and U_+ will rise. This causes U_a to rise even further until maximum output voltage (given by the power supply voltage) is reached

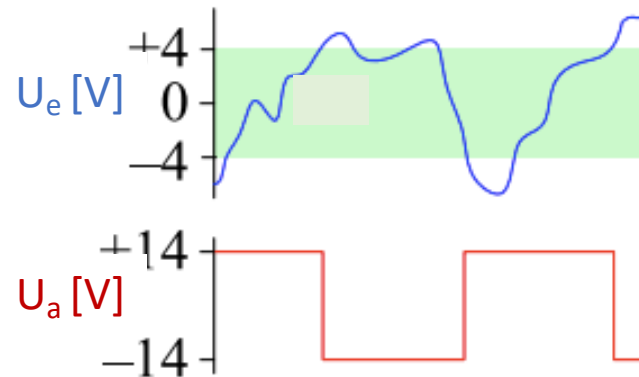Example: $U_{\max} = 14\text{V}$, $R_1 = 10\Omega$, $R_2 = 4\Omega$
If $U_a = 14\text{V}$, $U_+ = 4\text{V}$. If U_e exceeds 4V , $U_- > U_+$ and U_a flips to -14V





(3) Digital electronics

Digital electronics

Work with only two **voltage levels** (depend on type and input/output)

- High: 1, typically 2-5V
- Low : 0, typically 0-1.5V


○ **Hexadecimal 4-bit groups:**

0000	0	0100	4	1000	8	1100	C
0001	1	0101	5	1001	9	1101	D
0010	2	0110	6	1010	A	1110	E
0011	3	0111	7	1011	B	1111	F

Example:

- Decimal: 2022
- Binary: 0000 0111 1110 0110
- Hexadecimal: 07E6

○ **Boolean algebra**

 

AND OR

x	y	$x \wedge y$	$x \vee y$
0	0	0	0
1	0	0	1
0	1	0	1
1	1	1	1

NOT







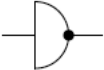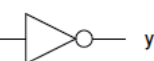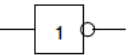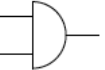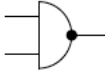
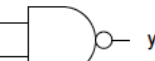

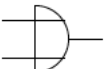
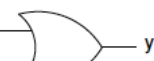
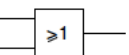
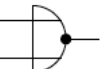

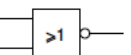
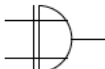

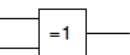
x	$\neg x$
0	1
1	0

Laws:


- Associativity
- Commutativity
- Distributivity

Logical operations


Full table of symbols, including secondary operations

 <p>Inverter $y = \bar{x}$</p> <p>x  y</p> <table border="1" data-bbox="343 523 459 620"> <thead> <tr> <th>x</th> <th>y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> </tr> </tbody> </table> <p></p>	x	y	0	1	1	0	 <p>AND $y = x_1 \cdot x_2$</p> <p>x_1 x_2  y</p> <table border="1" data-bbox="697 511 846 656"> <thead> <tr> <th>x_1</th> <th>x_2</th> <th>y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table> <p></p>	x_1	x_2	y	0	0	0	0	1	0	1	0	0	1	1	1	 <p>NAND $y = \overline{x_1 \cdot x_2}$</p> <p>$x_1$ x_2  y</p> <table border="1" data-bbox="1083 511 1232 656"> <thead> <tr> <th>x_1</th> <th>x_2</th> <th>y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table> <p></p>	x_1	x_2	y	0	0	1	0	1	1	1	0	1	1	1	0									
x	y																																														
0	1																																														
1	0																																														
x_1	x_2	y																																													
0	0	0																																													
0	1	0																																													
1	0	0																																													
1	1	1																																													
x_1	x_2	y																																													
0	0	1																																													
0	1	1																																													
1	0	1																																													
1	1	0																																													
 <p>OR $y = x_1 + x_2$</p> <p>x_1 x_2  y</p> <table border="1" data-bbox="324 783 459 928"> <thead> <tr> <th>x_1</th> <th>x_2</th> <th>y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table> <p></p>	x_1	x_2	y	0	0	0	0	1	1	1	0	1	1	1	1	 <p>NOR $y = \overline{x_1 + x_2}$</p> <p>x_1 x_2  y</p> <table border="1" data-bbox="697 783 846 928"> <thead> <tr> <th>x_1</th> <th>x_2</th> <th>y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table> <p></p>	x_1	x_2	y	0	0	1	0	1	0	1	0	0	1	1	0	 <p>EXOR $y = x_1 \oplus x_2$</p> <p>x_1 x_2  y</p> <table border="1" data-bbox="1083 783 1232 928"> <thead> <tr> <th>x_1</th> <th>x_2</th> <th>y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table> <p></p>	x_1	x_2	y	0	0	0	0	1	1	1	0	1	1	1	0
x_1	x_2	y																																													
0	0	0																																													
0	1	1																																													
1	0	1																																													
1	1	1																																													
x_1	x_2	y																																													
0	0	1																																													
0	1	0																																													
1	0	0																																													
1	1	0																																													
x_1	x_2	y																																													
0	0	0																																													
0	1	1																																													
1	0	1																																													
1	1	0																																													

Simple diode-based
AND gate

 


CMOS-based NAND gate

 

Flip Flop: SR latch

Flip flops (latches) are digital circuits with two stable states → store information



Simple SR Latch

 

Flip Flop: SR latch

Flip flops (latches) are digital circuits with two stable states → store information



Simple SR Latch

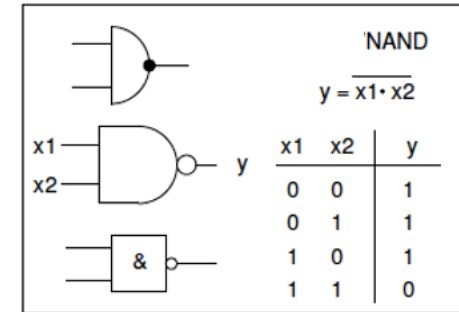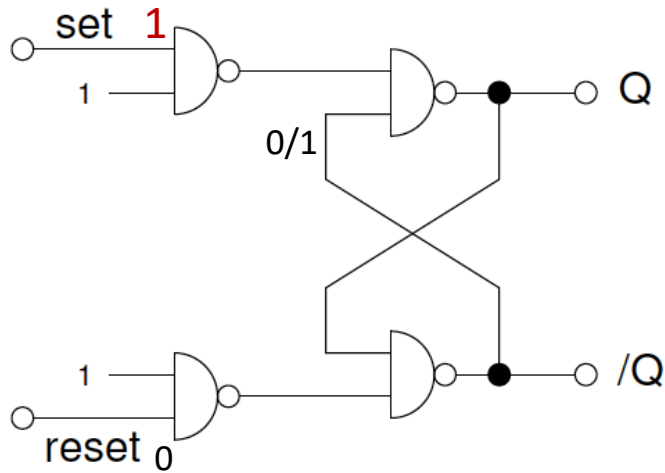

Flip Flop: SR latch

Flip flops (latches) are digital circuits with two stable states → store information



Simple SR Latch

 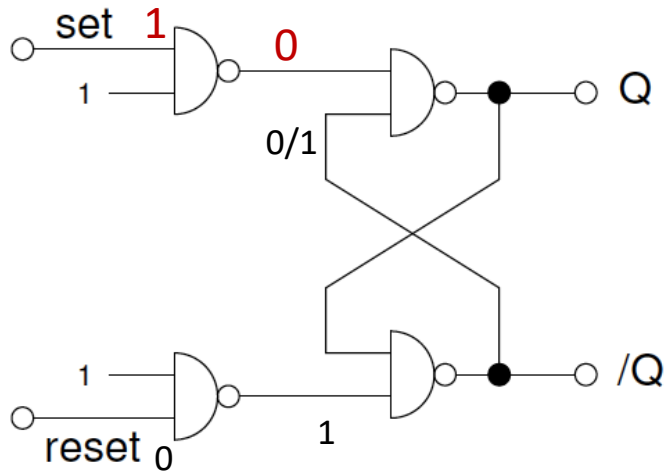

Flip Flop: SR latch

Flip flops (latches) are digital circuits with two stable states → store information



Simple SR Latch

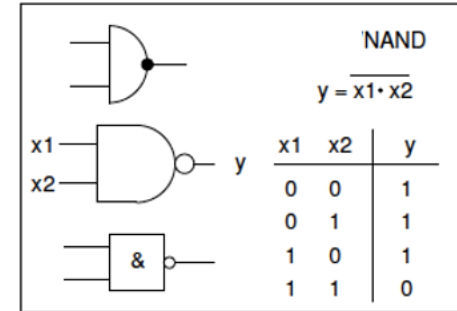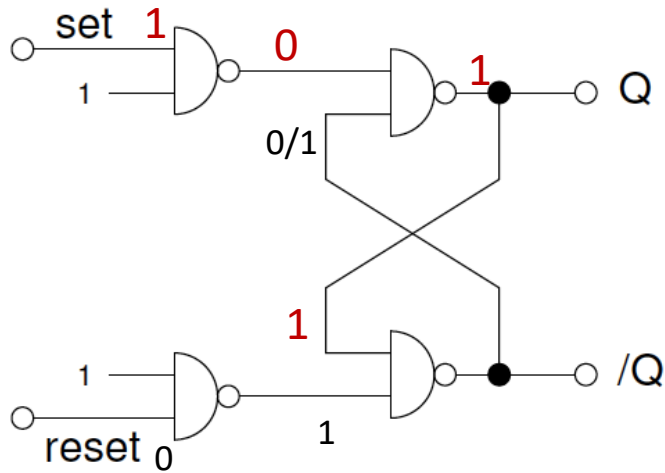

Flip Flop: SR latch

Flip flops (latches) are digital circuits with two stable states → store information


Simple SR Latch

 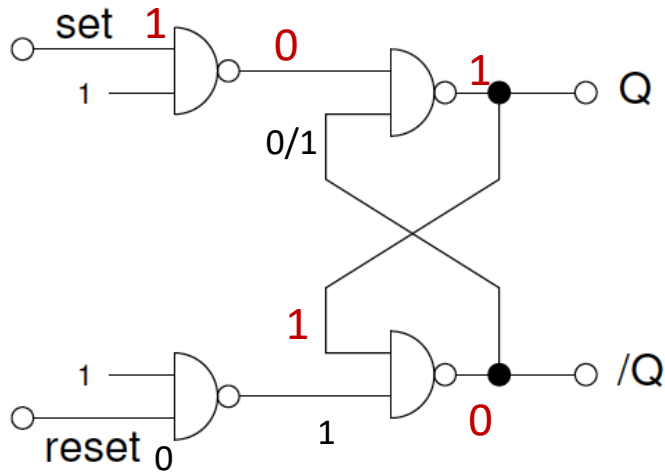


Flip Flop: SR latch

Flip flops (latches) are digital circuits with two stable states → store information

Simple SR Latch

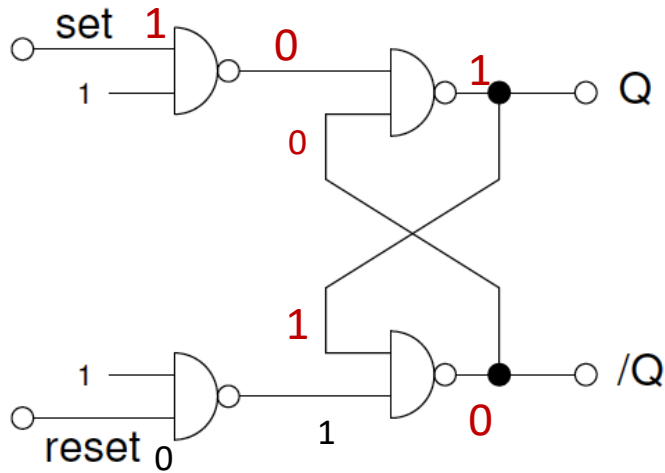


stable situation

 


Flip Flop: SR latch

Flip flops (latches) are digital circuits with two stable states → store information

Simple SR Latch

 

stable situation

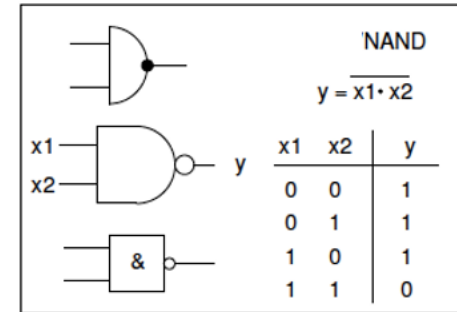

Likewise, setting the reset to 1 and the set to 0, will lead to the inverse stable situation


If the second inputs are 0, Q does not change latch is “opaque”

→ Gated or clocked SR latch


Flip Flop: SR latch

Flip flops (latches) are digital circuits with two stable states → store information

Simple SR Latch

 

Clocked SR Latch

 


clk provides "1" in a clocked way


D-latch and serial register

Flip flops (latches) are digital circuits with two stable states → store information

 D- Latch: only “set” input needed, due to **inverter**



symbol:

 


Truth table:

C	D	Q	\bar{Q}	Comment
0	X	Q_{prev}	\bar{Q}_{prev}	No change
1	0	0	1	Reset
1	1	1	0	Set


D-latch and serial register

Flip flops (latches) are digital circuits with two stable states → store information

 
D- Latch: only “set” input needed, due to **inverter**



symbol:

 

 
.... can be used to construct **serial shift register**




D-latch and serial register

Flip flops (latches) are digital circuits with two stable states → store information

 
D- Latch: only “set” input needed, due to **inverter**



symbol:

 

 
.... can be used to construct **serial shift register**




D-latch and serial register

Flip flops (latches) are digital circuits with two stable states → store information

 
D- Latch: only “set” input needed, due to **inverter**



symbol:

 

 
.... can be used to construct **serial shift register**




D-latch and serial register

Flip flops (latches) are digital circuits with two stable states → store information

 
D- Latch: only “set” input needed, due to **inverter**



symbol:

 

 .... can be used to construct **serial shift register**





(4) Circuit analysis, topologies


Circuit analysis

Basic circuit analysis can be performed based on the two Kirchhoff laws:

Junction rule or Kirchhoff's Current Law (KCL):

The currents flowing out of any closed
Region of a circuit sum to 0


$$\sum_{k=1}^n I_k = 0$$

 

Loop rule or Kirchhoff's Voltage Law (KVL):

The sum of voltage changes around
a closed loop is 0

$$\sum_{k=1}^n U_k = 0$$

 

How can we apply these laws to calculate the circuits in an efficient way ?


Circuit analysis

Basic circuit analysis can be performed based on the two Kirchhoff laws:

Junction rule or Kirchhoff's Current Law (KCL):

The currents flowing out of any closed Region of a circuit sum to 0


$$\sum_{k=1}^n I_k = 0$$

 

Loop rule or Kirchhoff's Voltage Law (KVL):

The sum of voltage changes around a closed loop is 0

$$\sum_{k=1}^n U_k = 0$$

 

How can we apply these laws to calculate the circuits in an efficient way ?

- Nodal analysis: identify nodes and applies KCL for each node
- Mesh current analysis: identify essential meshes, assign mesh current and apply KVL
- Thevenin equivalent: replace part of the network by source + resistance in series
- Norton equivalent: replace part of the network by source and resistance in parallel


Nodal Analysis

Node: section of the circuit which connects components.

Aim: determine the voltage at each node relative to a reference node, then use them to derive the other relevant quantities

Steps:

 - Identify all nodes and assign voltage variables (treat floating or dependent sources as super nodes with internal equation)
- Choose reference node
- Write a KCL equation at each node
- Solve the system of equations (e.g. via matrix inversion)



Nodal Analysis

Node: section of the circuit which connects components.

Aim: determine the voltage at each node relative to a reference node, then use them to derive the other relevant quantities

Steps:


- Identify all nodes and assign voltage variables (treat floating or dependent sources as super nodes with internal equation)
- Choose reference node
- Write a KCL equation at each node
- Solve the system of equations (e.g. via matrix inversion)

Example: $U_0: U_0 = 0V$

$U_1: U_1 = U$

$$U_2 \text{ KCL: } \frac{U_1 - U_2}{R_1} = \frac{U_2 - U_0}{R_4} + \frac{U_2 - U_3}{R_2}$$
 
$$U_3 \text{ KCL: } \frac{U_2 - U_3}{R_2} = \frac{U_3 - U_0}{R_3}$$




Nodal Analysis

Node: section of the circuit which connects components.

Aim: determine the voltage at each node relative to a reference node, then use them to derive the other relevant quantities

Steps:

 - Identify all nodes and assign voltage variables (treat floating or dependent sources as super nodes with internal equation)
- Choose reference node
- Write a KCL equation at each node
- Solve the system of equations (e.g. via matrix inversion)



Example: $U_0: U_0 = 0V$

$U_1: U_1 = U$

U_2 KCL: $\frac{U_1 - U_2}{R_1} = \frac{U_2 - U_0}{R_4} + \frac{U_2 - U_3}{R_2}$

U_3 KCL: $\frac{U_2 - U_3}{R_2} = \frac{U_3 - U_0}{R_3}$

- conveniently using conductance $G = \frac{1}{R}$ -

$$\rightarrow \begin{bmatrix} G_1 + G_2 + G_4 & -G_2 \\ G_2 & -G_2 - G_3 \end{bmatrix} \begin{pmatrix} U_2 \\ U_3 \end{pmatrix} = \begin{pmatrix} G_1 U \\ 0 \end{pmatrix}$$

- invert matrix or solve by substitution -

$$\rightarrow U_3 = \frac{G_1 G_2 U}{G_2(G_1 + G_4) + G_3(G_1 + G_2 + G_4)} \rightarrow U_2$$

Mesh current Analysis


Essential mesh: loop in the circuit that does not contain any other loop.

Aim: determine the current through each mesh

then use them to derive the other relevant quantities

Steps:

 - Identify all essential meshes and assign mesh current (special treatment for dependent sources and current sources which are part of two meshes)
- Apply the KVL for each mesh
- Solve the system of equations (e.g. via matrix inversion)



Mesh current Analysis

Essential mesh: loop in the circuit that does not contain any other loop.

Aim: determine the current through each mesh


then use them to derive the other relevant quantities

Steps:

- Identify all essential meshes and assign mesh current (special treatment for dependent sources and current sources which are part of two meshes)
- Apply the KVL for each mesh
- Solve the system of equations (e.g. via matrix inversion)

 Example: Mesh 1: $R_1 I_1 + R_4 (I_1 - I_2) = U$

Mesh 2: $R_4 (I_2 - I_1) + R_2 I_2 + R_3 I_2 = 0$



Mesh current Analysis


Essential mesh: loop in the circuit that does not contain any other loop.

Aim: determine the current through each mesh

then use them to derive the other relevant quantities

Steps:

 - Identify all essential meshes and assign mesh current (special treatment for dependent sources and current sources which are part of two meshes)
- Apply the KVL for each mesh
- Solve the system of equations (e.g. via matrix inversion)



Example: Mesh 1: $R_1 I_1 + R_4 (I_1 - I_2) = U$
Mesh 2: $R_4 (I_2 - I_1) + R_2 I_2 + R_3 I_2 = 0$

$$\rightarrow \begin{bmatrix} R_1 + R_4 & -R_4 \\ -R_4 & R_2 + R_3 + R_4 \end{bmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} U \\ 0 \end{pmatrix}$$


- invert matrix or solve by substitution -

$$\rightarrow I_1 = \frac{(R_2 + R_3 + R_4) U}{(R_1 + R_4)(R_2 + R_3 + R_4) - R_4^2} \rightarrow I_2$$

Thevenin equivalent circuit

Thevenin's theorem: Any linear circuit containing several voltages and resistances can be replaced by just one single voltage in series with a single resistance connected across the load"


Example circuit:

 


Thevenin equivalent circuit

Thevenin's theorem: Any linear circuit containing several voltages and resistances can be replaced by just one single voltage in series with a single resistance connected across the load“

Example circuit:

 

 Step1: remove load and shorten sources. Then calculate total Thevenin resistance R_T wrt A/B




$$R_T = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$


Thevenin equivalent circuit

Thevenin's theorem: Any linear circuit containing several voltages and resistances can be replaced by just one single voltage in series with a single resistance connected across the load"

Example circuit:

 


 Step1: remove load and shorten sources. Then calculate total Thevenin resistance R_T wrt A/B



$$R_T = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

 Step2: Reconnect sources. Calculate Thevenin voltage U_T




$$I = \frac{U_1 - U_2}{R_1 + R_2}$$

$$U_T = U_{AB} = U_1 - IR_1 = U_2 + IR_2$$

$$= \frac{R_1 U_2 + U_1 R_2}{R_1 + R_2}$$

 Example: nodal analysis

Revisiting Voltage divider biasing circuit



Reminder: The voltage U_B across R_2 forward-biases the BE junction

Here: can use **nodal analysis**:

Apply Kirchhoff's current law (KCL) at **node 2**


Reminder the $I_B - U_B$ relation does not follow Ohms law but a diode-like input characteristics (which for this exercise, we pretend not to know)

$$U1: \quad U_1 = U_0 \quad (1)$$

$$U2 \text{ KCL: } I_1 = I_2 + I_B \quad (2)$$

 Example: nodal analysis

Revisiting Voltage divider biasing circuit



Reminder: The voltage U_B across R_2 forward-biases the BE junction

Here: can use **nodal analysis**:

Apply Kirchhoff's current law (KCL) at **node 2**

Reminder the $I_B - U_B$ relation does not follow Ohms law but a diode-like input characteristics (which for this exercise, we pretend not to know)

$$U_1: \quad U_1 = U_0 \quad (1)$$

$$U_2 \text{ KCL: } I_1 = I_2 + I_B \quad (2)$$


$$(1) \ \& \ (2) \ \Rightarrow \frac{U_0 - U_B}{R_1} = \frac{U_B}{R_2} + I_B \ \Rightarrow \ U_0 - U_B = U_B \frac{R_1}{R_2} + I_B R_1 \ \Rightarrow \ U_B \frac{R_1 + R_2}{R_2} = U_0 - I_B R_1$$

$$\Rightarrow U_B = U_0 \frac{R_2}{R_1 + R_2} - I_B \frac{R_1 R_2}{R_1 + R_2}$$

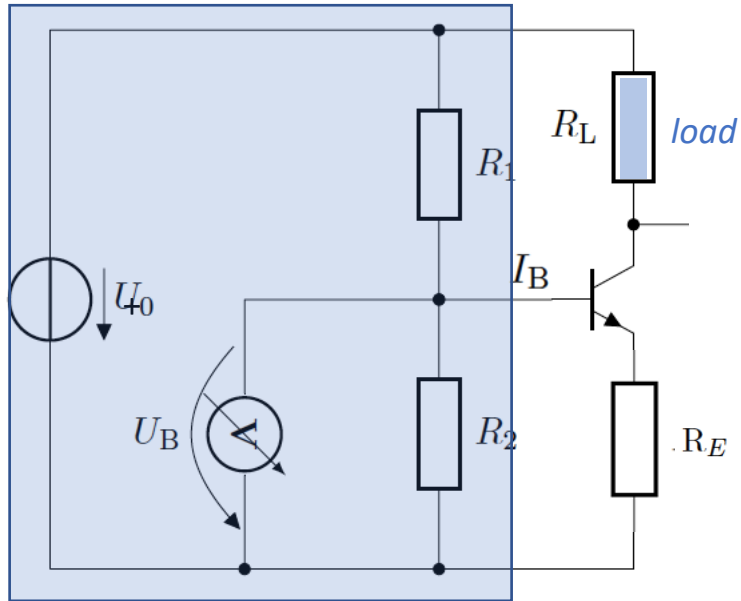Example: Thevenin equivalent

Voltage divider biasing with emitter resistance

Reminder: We can stabilize the working point by adding an emitter resistance




In order to simplify the calculations, we want to replace the voltage divider by the Thevenin equivalent

- Thevenin voltage: $U_T = U_0 \frac{R_2}{R_1 + R_2}$
- Thevenin resistance: $R_T = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$

 Example: Thevenin equivalent

Voltage divider biasing with emitter resistance

Reminder: We can stabilize the working point by adding an emitter resistance



In order to simplify the calculations, we want to replace the voltage divider by the Thevenin equivalent


- Thevenin voltage: $U_T = U_0 \frac{R_2}{R_1 + R_2}$

- Thevenin resistance: $R_T = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$

 Example: Thevenin equivalent

Voltage divider biasing with emitter resistance

Reminder: We can stabilize the working point by adding an emitter resistance



In order to simplify the calculations, we want to replace the voltage divider by the Thevenin equivalent

- Thevenin voltage: $U_T = U_0 \frac{R_2}{R_1 + R_2}$


- Thevenin resistance: $R_T = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$

Now we can analyze the mesh (KVL):

$$U_T = I_B R_T + U_{BE} + R_E (I_B + I_C)$$

 Example: Thevenin equivalent

Voltage divider biasing with emitter resistance



Reminder: We can stabilize the working point by adding an emitter resistance

In order to simplify the calculations, we want to replace the voltage divider by the Thevenin equivalent

- Thevenin voltage: $U_T = U_0 \frac{R_2}{R_1 + R_2}$

- Thevenin resistance: $R_T = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$

Now we can analyze the mesh (KVL):

$$U_T = I_B R_T + U_{BE} + R_E (I_B + I_C)$$

with $I_C = \beta I_B$ (transfer characteristics):

$$U_T = I_B R_T + U_{BE} + R_E I_B (1 + \beta)$$

$$\rightarrow I_B = \frac{U_T - U_{BE}}{R_T + R_E (1 + \beta)} \rightarrow I_C = \beta I_B \rightarrow \dots$$



Circuit topologies

The formal layout of the equations following the application of Kirchhoff's rules applied to a circuit does not depend on the type of device connected in the branches. It only depends on the topology of the circuit.

Circuit Topology describes how components in a network are connected. Circuits with different physical layout can have the same topology.

Example: three circuits with the same topology:

  Example: There are only two topologies for a network with 2 branches: series and parallel.




Graph theory

Mathematical **Graph theory** is used to analyze the topology:


Graphs represent the aspects of a network connected to its topology. The devices are left out.

→ a line represents a device. A node represents all points at the same potential.

Example: **circuit**

 

graph

 

The graph representation makes it easier to analyze complex circuits.


Graphs are **equivalent** if they can be transformed into each other by translation, rotation, reflection, stretching or crossing/knotting the branches,

Graph theory: dual graph

Each graph has a **dual graph** with the following elements exchanged:

- $R \leftrightarrow 1/R$
- $L \leftrightarrow C$
- $U \leftrightarrow I$
- $U \text{ source} \leftrightarrow I \text{ source}$
- $\text{mesh} \leftrightarrow \text{node}$

graph

 


$$I_3 = -I_1 - I_2 = U \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

Graph theory: dual graph

Each graph has a **dual graph** with the following elements exchanged:

 - $R \leftrightarrow 1/R$
- $L \leftrightarrow C$
- $U \leftrightarrow I$
- $U \text{ source} \leftrightarrow I \text{ source}$
- $\text{mesh} \leftrightarrow \text{node} \bullet$




$$I_3 = -I_1 - I_2 = U \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

Graph theory: dual graph

Each graph has a **dual graph** with the following elements exchanged:

 - $R \leftrightarrow 1/R$
- $L \leftrightarrow C$
- $U \leftrightarrow I$
- $U \text{ source} \leftrightarrow I \text{ source}$
- $\text{mesh} \leftrightarrow \text{node}$




converted parallel circuit into serial circuit

$$I_3 = -I_1 - I_2 = U \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

Graph theory: dual graph

Each graph has a **dual graph** with the following elements exchanged:

 - $R \leftrightarrow 1/R$
- $L \leftrightarrow C$
- $U \leftrightarrow I$
- $U \text{ source} \leftrightarrow I \text{ source}$
- $\text{mesh} \leftrightarrow \text{node}$



converted parallel circuit into serial circuit

both solutions are equivalent as $U \leftrightarrow I$

$$I_3 = -I_1 - I_2 = U \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$u_3 - u_1 = I(r_1 + r_2) = I \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

Introduction into Electronics

- (1) Reminder: Electrical circuits
- (2) Analog electronics
- (3) Digital electronics
- (4) Circuit analysis, circuit topologies

